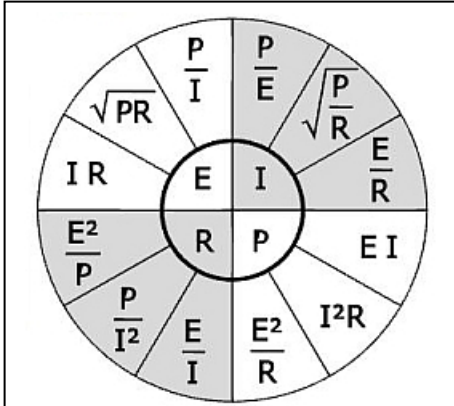



[1]



Analyzing circuits (a) and (b)


Series Circuit:

Total Resistance	$R_1+R_2+R_3+R_4$	= 100 Ohms
Circuit Current:	$E/R_{total} = I$	= 12/100 = .12 Amperes
Circuit Power:	$E \times I = P$	= 12 x .12 = 1.44 Watts
Volts across R1:	$I \times R_1$	= .12 x 10 = 1.2 Volts
Volts across R2:	$I \times R_2$	= .12 x 20 = 2.4 Volts
Volts across R3:	$I \times R_3$	= .12 x 30 = 3.6 Volts
Volts across R4:	$I \times R_4$	= .12 x 40 = 4.8 Volts
Power in R1	$E_1 \times I$	= 1.2 x .12 = .144 Watts
Power in R2	$E_2 \times I$	= 2.4 x .12 = .288 Watts
Power in R3	$E_3 \times I$	= 3.6 x .12 = .423 Watts
Power in R4	$E_4 \times I$	= 4.8 x .12 = .576 Watts

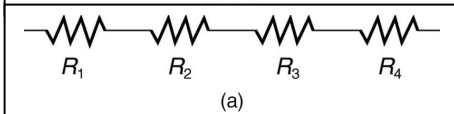



Parallel Circuit:

Total Resistance	$1/R_1+1/R_2+1/R_3+1/R_4 = 1/R_{total}$	
Current thru R1:	E/R_1	= 12/10 = 1.2 Amperes
Current thru R2:	E/R_2	= 12/20 = 0.6 Amperes
Current thru R3:	E/R_3	= 12/30 = 0.4 Amperes
Current thru R4:	E/R_4	= 12/40 = 0.3 Amperes
Circuit Current:	$I_1 + I_2 + I_3 + I_4$	= 2.5 Amperes
Circuit Power	$E \times I_T$	= 12 x 2.5 = 30 Watts
Power in R1:	$E \times I_1$	= 12 x 1.2 = 14.4 Watts
Power in R2:	$E \times I_2$	= 12 x .6 = 7.2 Watts
Power in R3:	$E \times I_3$	= 12 x .4 = 4.8 Watts
Power in R4:	$E \times I_4$	= 12 x .3 = 3.6 Watts

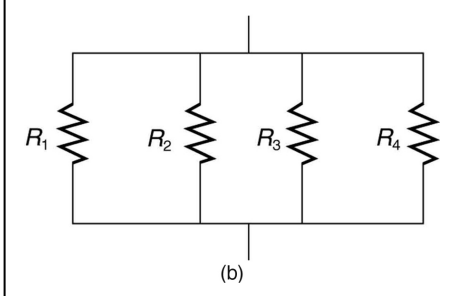

R1 = 10 Ohms R3 = 30 Ohms
 R2 = 20 Ohms R4 = 40 Ohms
 Each circuit connects to 12Volts

[2]

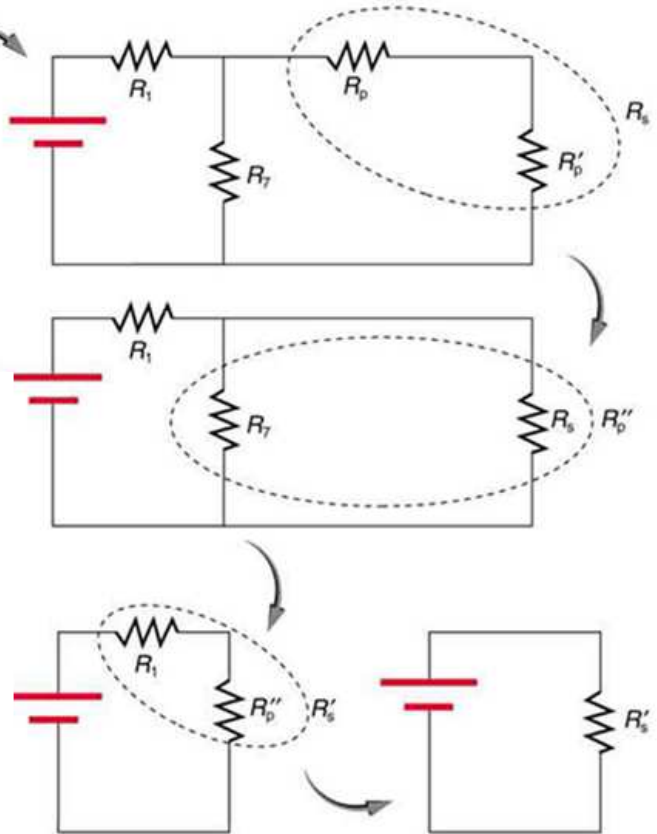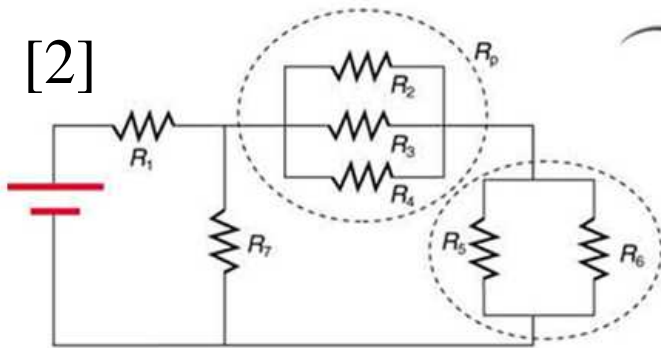

1. Cover the answers to the circuit analysis at the top of this page. Do all the calculations yourself. Find the implanted error.

2. All values in this multi-resistor circuit are 20 Ohms. Moving clockwise, a step at a time, reduce this multi-resistor circuit to 4, then 3, 2 and finally to 1 resistor which represents the series-parallel resistance of the circuit. Use the series and parallel resistor formulae from IS-4 to solve. Did you discover the short cut?

K6SQN